

Computer Science: An Overview
Edition 8 Activities
Chapter 1, Data Storage
Lab 1: Digital Gates
Part B – Flip-flops

Lab Report

Date _____

Name _____

Section _____


Procedure

Start the LogicGates applet and carry out the instructions below. This lab will cover the flip-flop circuits from Chapter 1 that store single bits.

A flip flop is memory circuit that stores one bit. These circuits can be set to 0 or 1 and retain their values despite some changes to their input.

Stage 1. A non-erasable circuit


In this stage we will start with a circuit that is not a flip-flop, but illustrates a circuit that remembers if it has ever been set to an output of 1. It has an output of 0 until its single input is 1 – then, after that, its output remains 1 even if the input is changed back to 0. This is a *non-erasable* circuit – you can write a 1 value into it once, but having done so, you can't change it. Note that in this circuit one connector goes over the OR gate, which is ok.

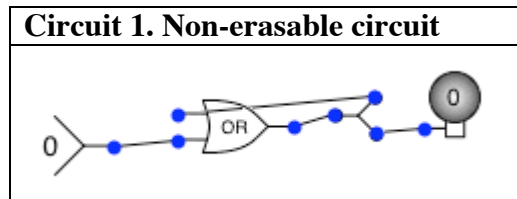

Build this circuit and then run it, setting the input to 1. What happens? Then reset the input back to 0 and try it. What happens now? Describe what happens and explain why the circuit remains at 1 despite changes to its input.

Stage 2. An OR/AND/NOT flip-flop

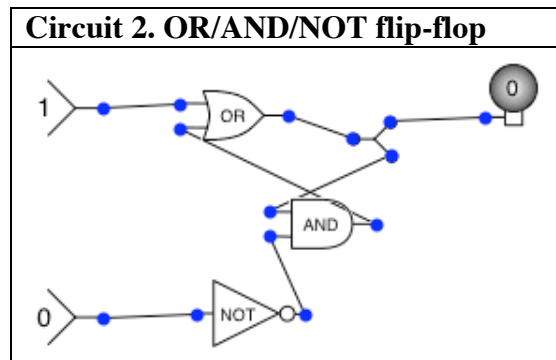In this stage you will test the flip-flop circuit from Figure 1.4 on page 23. Build this circuit.



A. Set the lower input to 1 and then change the upper input back and front between 0 and 1. What happens to the output?

B. First set the lower input to 1 and the upper input to 0. The output light should be 0. Now set the lower input to 0 so you should have upper as 1, lower as 0.

1. What is the value of the output? _____


2. What happens when you switch the upper input from 0 to 1?

3. What happens when you switch the upper input back from 1 to 0?

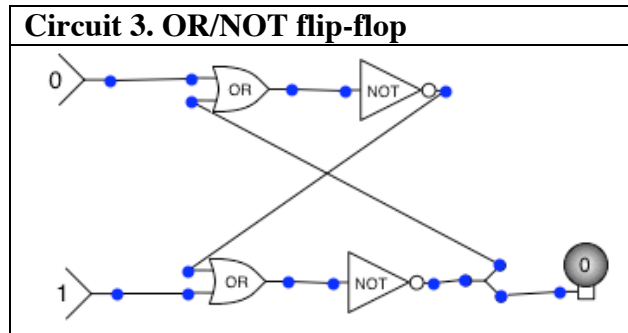4. What is the similarity between this flip-flop and the Non-erasable circuit in Stage 1?

Stage 2. An OR/AND flip-flop

In this stage you will test the flip-flop circuit from Figure 1.5 on page 24. Build the circuit below.



Now investigate this circuit to figure out how it works.

What happens when you hold the lower input to 0 and change the upper input?

What happens when you hold the lower input to 1 and change the upper input?

How does this flip-flop work? Does it work exactly the same as the OR/AND/NOT flip-flop?